
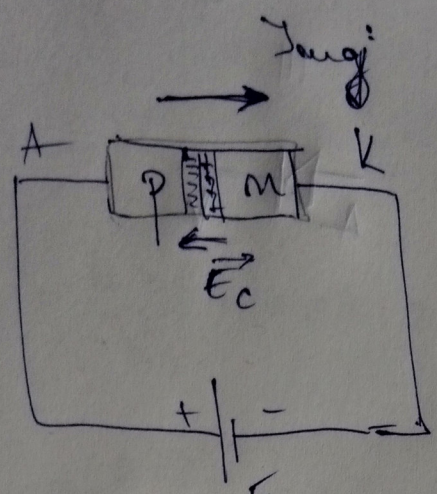






SEMINAR 2 ELECTRONICĂ II

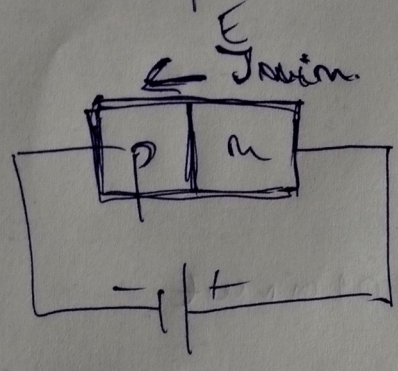


pol. directă
forward bias
F.B.



pol. inversă
reverse bias.
(R.B.V.)

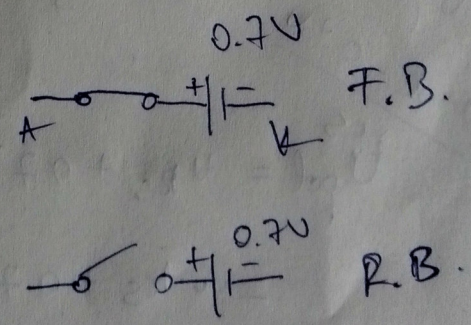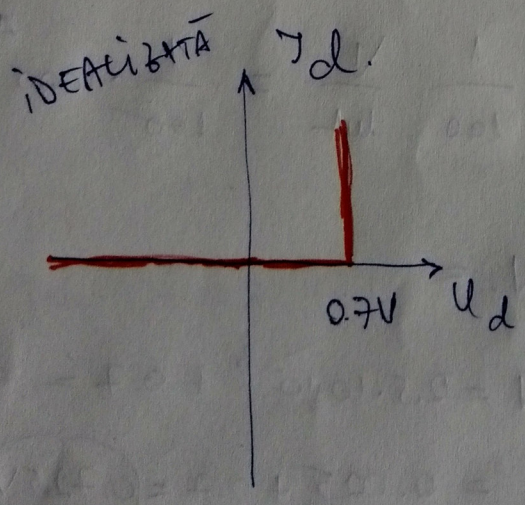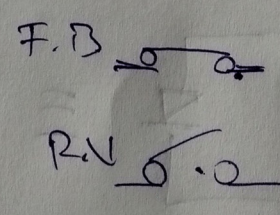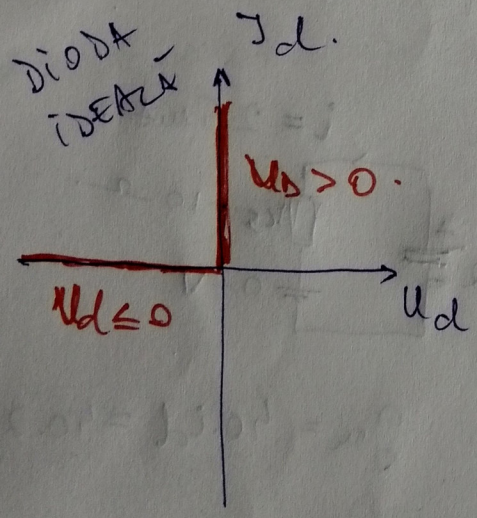

PRACTICAL
MODEL

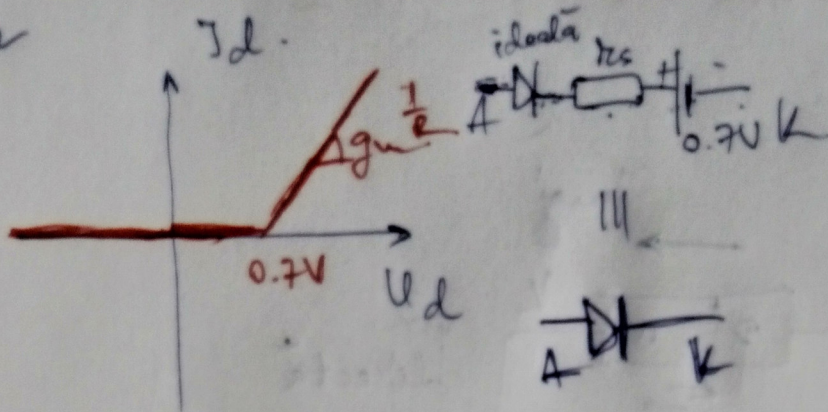


② $i_d = 2.5 \text{ mA}$

$U_d = 0.7V$

$u(t) = 10 \sin \omega t = 0.01 \sin \omega t$
mV

circuit de
polarizare

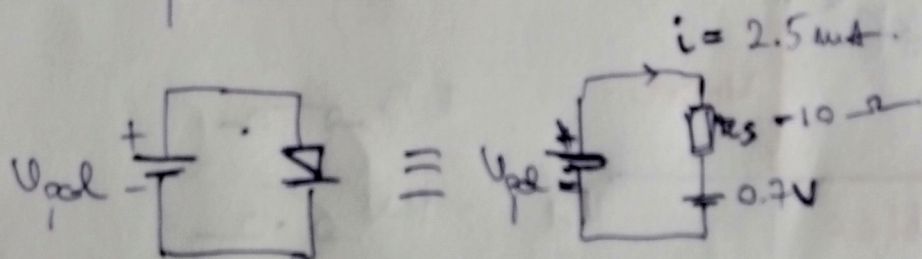$U_{pol} = U_{pol} + u(t)$
 $\begin{cases} 0.715V \\ 0.735V \end{cases}$



$g_m = 40 \cdot i_d = 40 \cdot 2.5 = 100 \text{ uA/V}$

$U_{pol} = i \cdot r_{ES} + 0.7V \Rightarrow$

$\Rightarrow i \cdot r_{ES} = U_{pol} - 0.7V$

$i = \frac{U_{pol} - 0.7V}{r_{ES}}$

$\Rightarrow r_{ES} = \frac{1}{100} \frac{V}{\text{mA}} = \frac{1}{100} \cdot 1000 \frac{V}{A} = 10 \Omega$

$U_{pol} = U_{RES} + 0.7V =$

$= i \cdot r_{ES} + 0.7V = 2.5 \cdot 10 \cdot 10^{-3} + 0.7 =$

$= 0.025 + 0.7 = 0.725V$

$$i' = \frac{U'_{\text{pel}}}{r_{\text{S}}} - 0.07.$$

$$i' = \frac{U'_{\text{pel}}}{10} - 0.07 = \frac{U_{\text{pel}}}{10} + \frac{u(t)}{10} - 0.07$$

$$i' = \frac{U'_{\text{pel}}}{r_{\text{S}}} - 0.07 = \frac{U'_{\text{pel}}}{10} - 0.07 = \frac{U_{\text{pel}}}{10} + \frac{u(t)}{10} - 0.07 =$$

$$= \frac{0.725}{10} - 0.07 + \frac{u(t)}{10} = 0.0725 - 0.07 + \frac{0.01 \sin \omega t}{10} =$$

$$= 0.0025 + 0.001 \sin \omega t \Rightarrow$$

$$\Rightarrow i' = 2.5 \text{ mA} + 1 \text{ mV} \sin \omega t \text{ mA}$$

$$U_{\text{pel}} = i r_{\text{S}} + 0.7 \text{ V} \Rightarrow i r_{\text{S}} = U_{\text{pel}} - 0.7$$

$$i = \frac{U_{\text{pel}} - 0.7}{r_{\text{S}}} = \frac{U_{\text{pel}} - 0.7}{10} \neq =$$

$$= \frac{0.035}{10} = 0.0035$$

↓
3.5 mA

$$100 \text{ mA} \sim 1 \text{ V}$$

$$x = 10 \text{ mV} (0.01 \text{ V})$$

$$x = 0.01 \cdot 100 = 1 \text{ mA}$$


$$g_m = 100 \text{ mA/V}$$

$$U = 10 \text{ V}$$


$$R = 1 \text{ k}\Omega$$

= 3 =

3. Tema

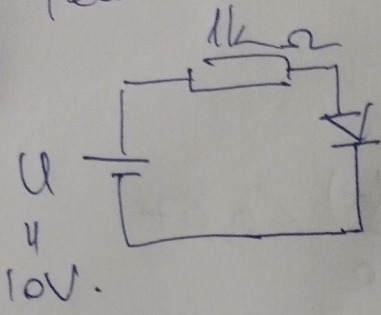




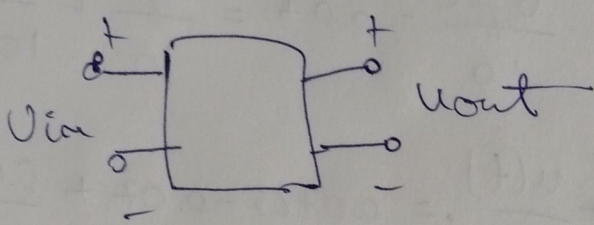
$\gamma = ?$ hint: modelul idealizat practic



$$\frac{U_{out}}{U_{in}} = f(U_{in})$$

Tema 5, b, c, d

4.

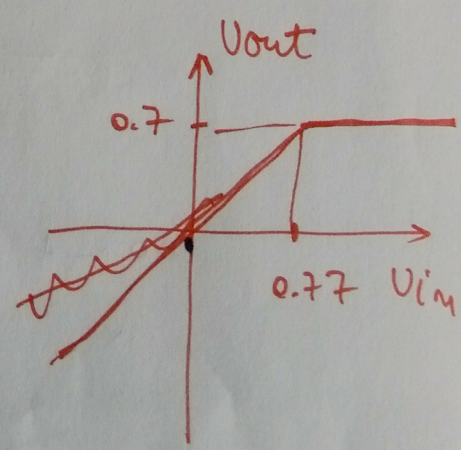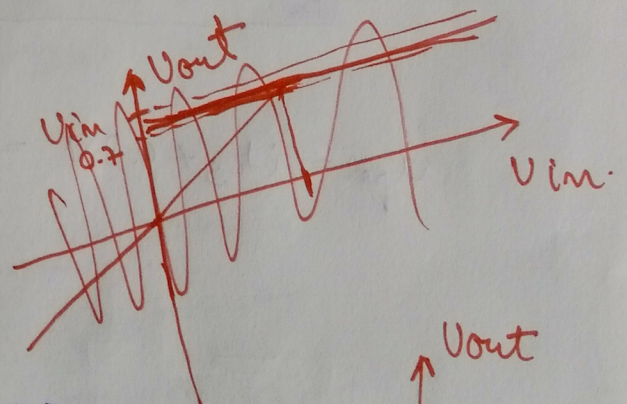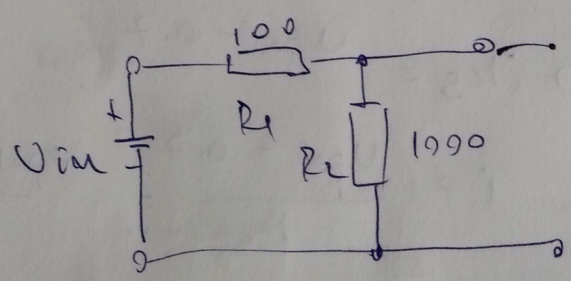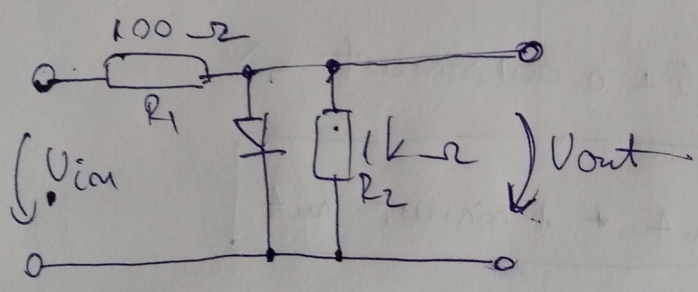


$$U_{in} = i \cdot 1100 = i \cdot R_1$$

$$U_{out} = i \cdot 1000 = i \cdot R_2$$

$$\frac{U_{out}}{U_{in}} = \frac{i \cdot 1000}{i \cdot 1100} = \frac{10}{11} = 0.91$$

$$U_{out} = 0.91 U_{in} \approx 0.7V$$



$$U_{out} = 0.7V$$

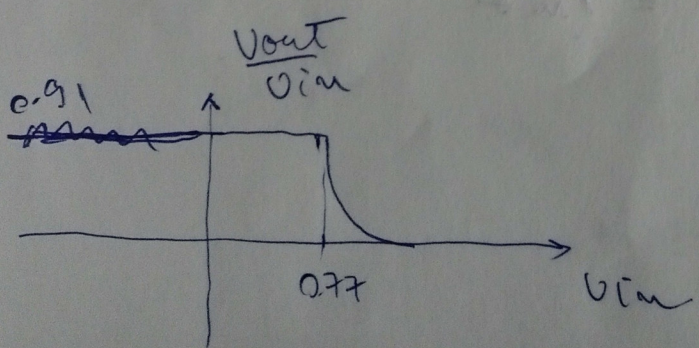


$$0.91 U_{in} = 0.7V$$

$$U_{in} = \frac{0.7}{0.91} = 0.77V$$

a)

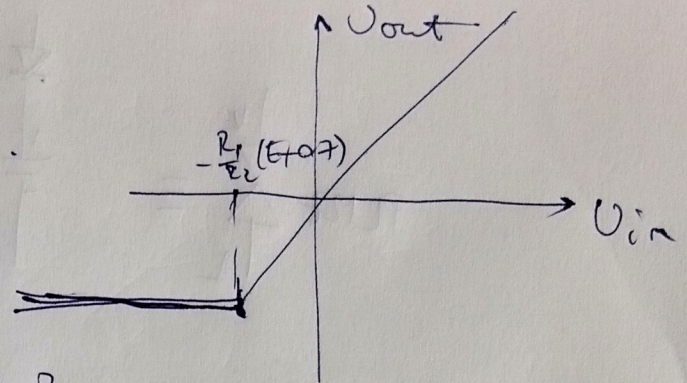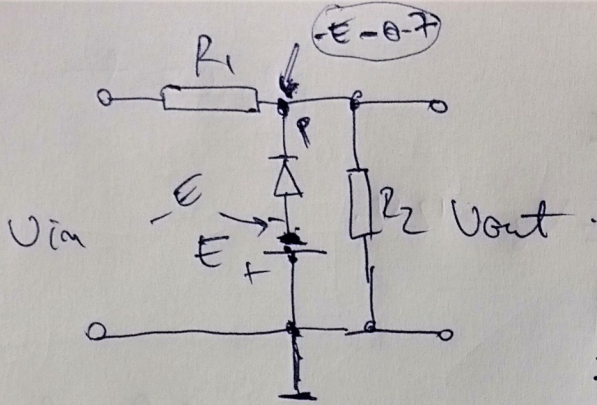


$V_p > 0.7V \equiv$

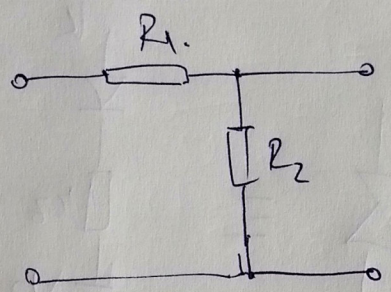




$V_{out} = \frac{R_2}{R_1} \cdot V_{in}$



$V_p = \frac{R_2}{R_1} \cdot V_{in}$

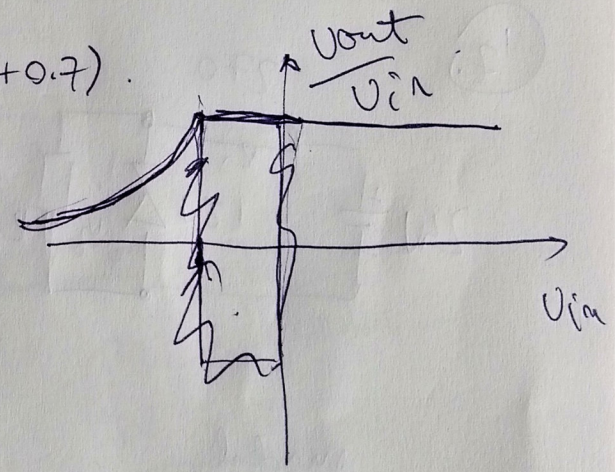$V_{in} = \frac{R_1}{R_2} \cdot V_p = -\frac{R_1}{R_2} (E+0.7)$




$V_{in} \geq -\frac{R_1}{R_2} (E+0.7)$

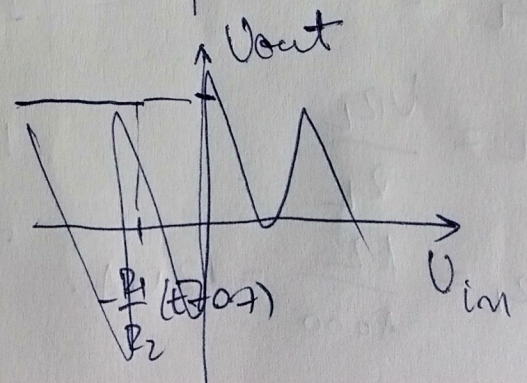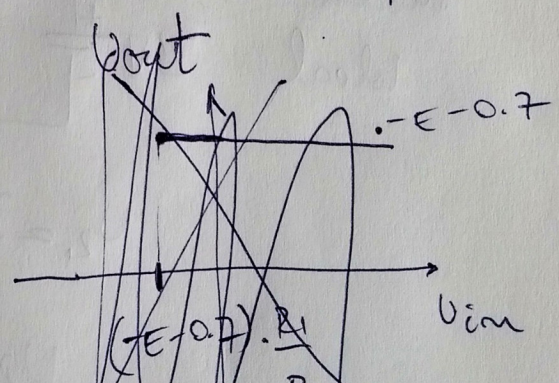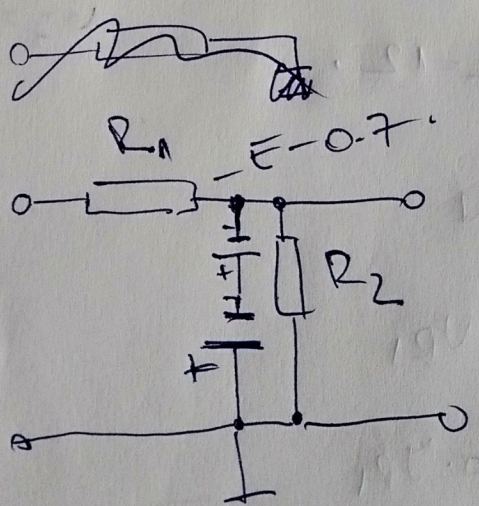

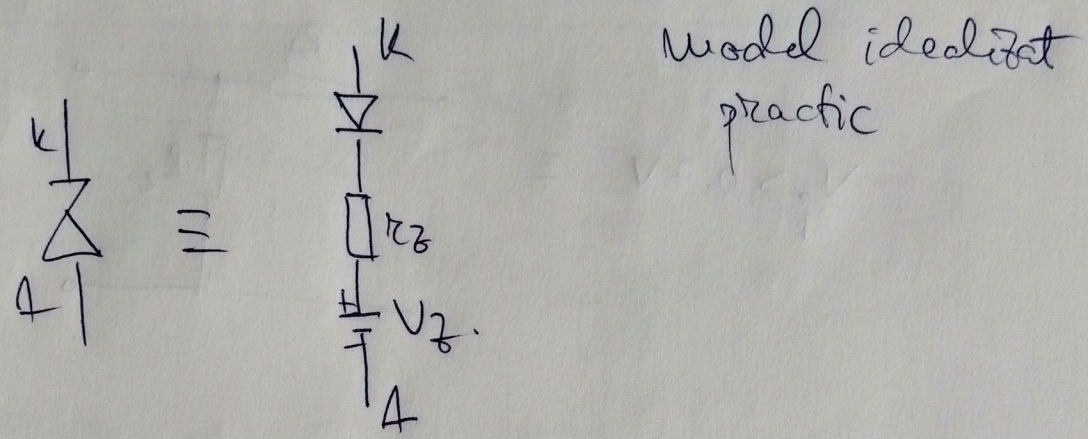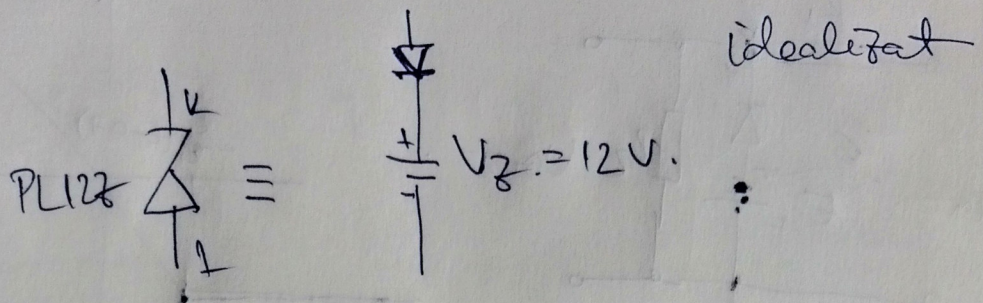

17.

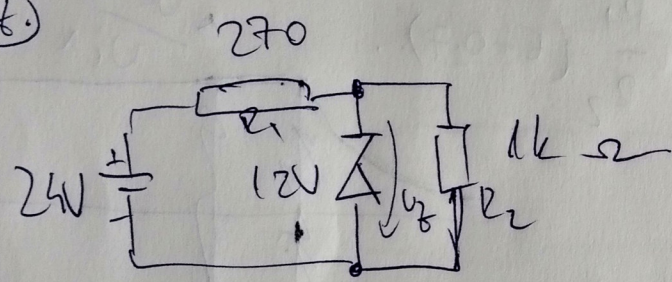


~~1000 / 270 = 3.7~~

$$24 = i \cdot 1270$$

$$U_z = i \cdot 1000$$

model ideal

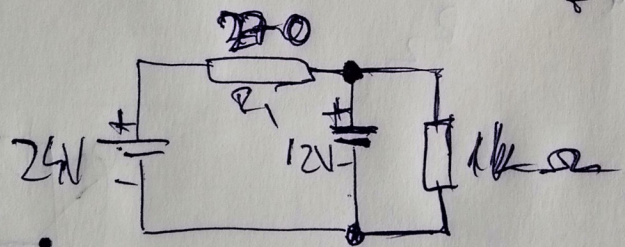

$$\frac{U_z}{24} = \frac{1000}{1270}$$

$$U_{R1} = 24 - 12 = 12$$

$$U_z = 24 \cdot \frac{1000}{1270} = 18.898V > 12V$$

$$U_{R1} = 12V$$

$$I_{R1} \cdot R_1 = U_{R1}$$


$$12 = 270 \cdot I_{R1}$$

$$U_{RL} = 12V$$

$$I_{RL} = \frac{U_{RL}}{R_L}$$

$$I_{RL} = \frac{12}{1000} = 12mA$$

$$I_{R1} = \frac{12}{270} = 44.4mA$$

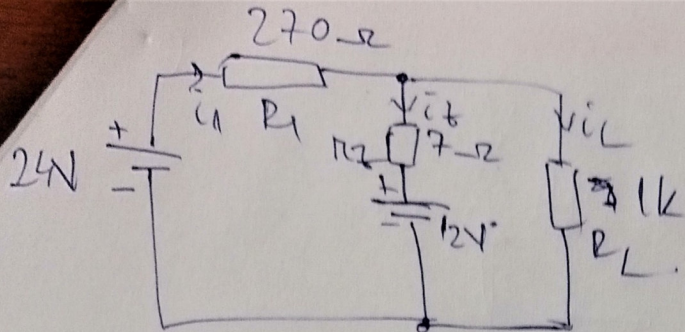

$$\left\{ \begin{array}{l} 24 = u_{R_1} + u_2 + 12 \\ 12 + u_2 = u_{R_L} \\ R_1 = i_2 + i_L \\ i_1 \end{array} \right. \Leftrightarrow \left\{ \begin{array}{l} \cancel{24} - \cancel{i_1 R_1} + i_2 24 = i_1 R_1 + i_2 R_2 + 12 \\ 12 + i_2 R_2 = i_L R_L \\ i_1 = i_2 + i_L \end{array} \right.$$

(71 + 72) Tema

CAB

$$u_2 = 16V$$

$$i_2 = 25mA$$

$$R_2 = 15\Omega$$

