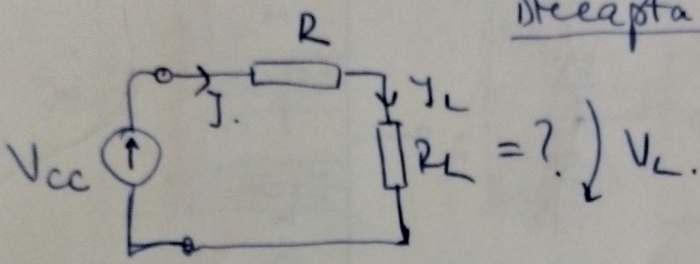



Încăputa de sarcină :



$$V_{cc} = I \cdot R + V_L$$


$$V_L = V_{cc} - I \cdot R$$



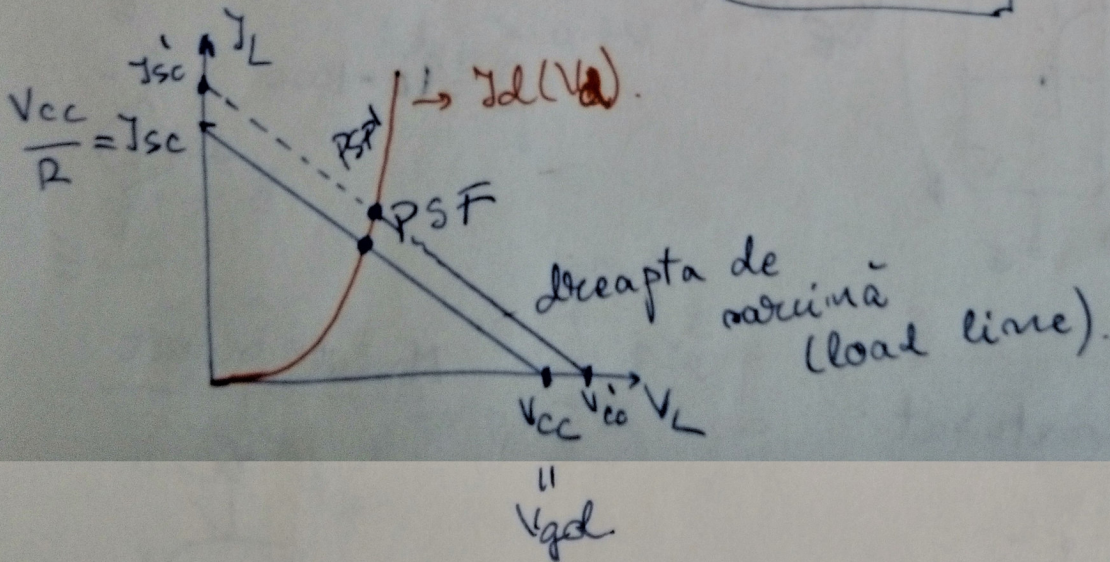
$$-I = \frac{V_L - V_{cc}}{R} \Rightarrow I = \frac{V_{cc} - V_L}{R} = I_{sc} - \frac{1}{R} \cdot V_L$$




Tranzistorul bipolar :

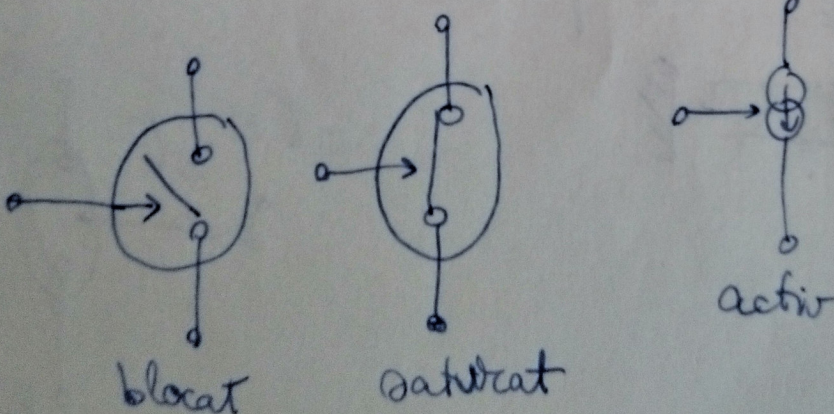- switch controlabil electronic (blocat/saturat)
- sursă de curent (activă)



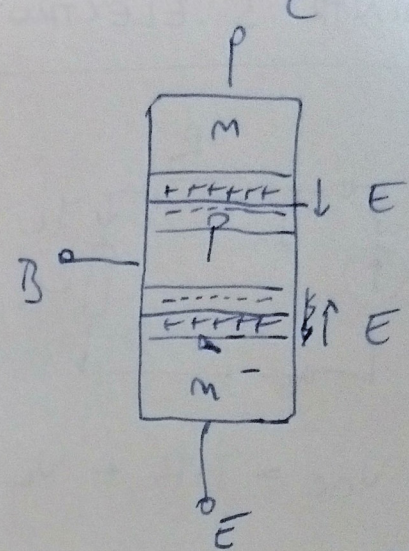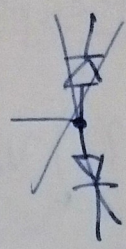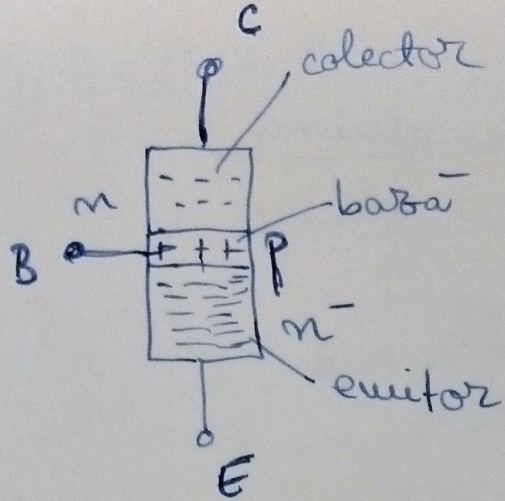


Modelul activ:

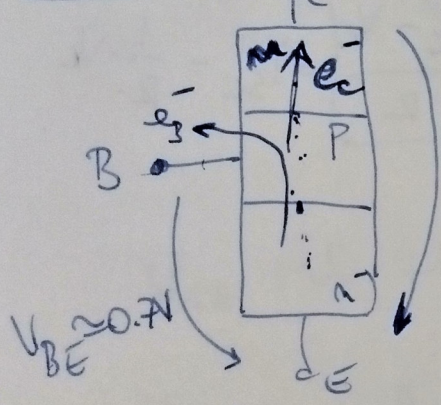


$V_{CE} \approx V$

$I_C = \beta \cdot I_B$

$\beta = 10 - 1000$


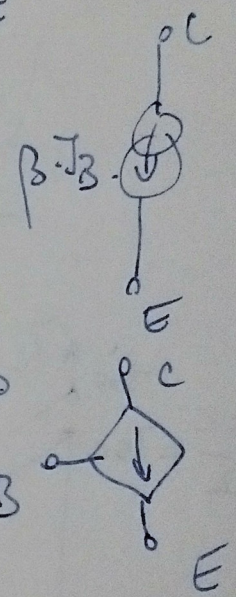


Modelul saturat:

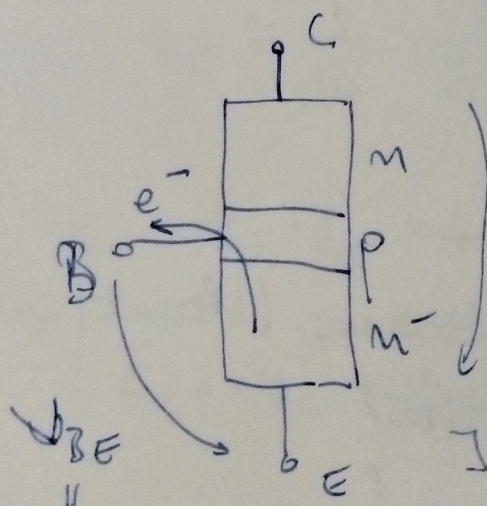


$V_{CE} \approx 0.2V$


$I_C < \beta \cdot I_B$

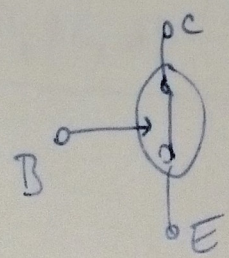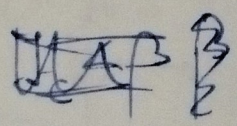


Modelul blocat

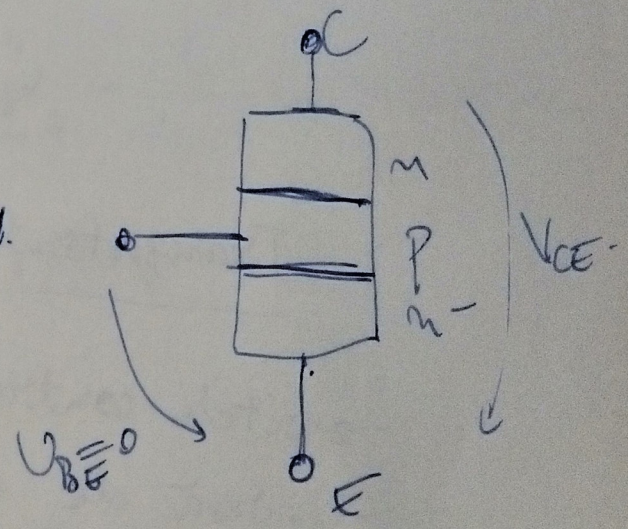


$V_{BE} = 0$

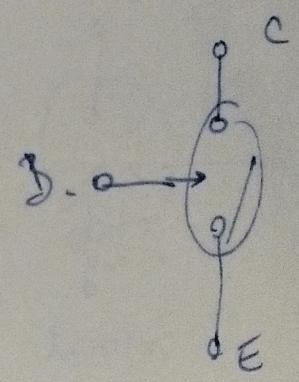

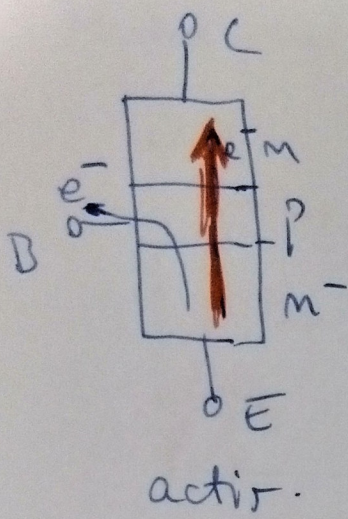


$$V_{CE} > 0$$

$$I_C \approx \beta \cdot I_B$$

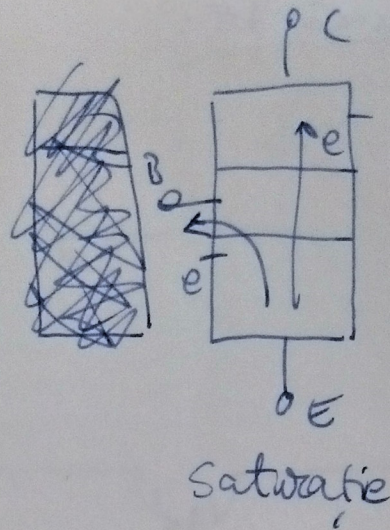

$$V_{CE} \approx 0 - 0.2V$$

$$I_C < \beta \cdot I_B$$

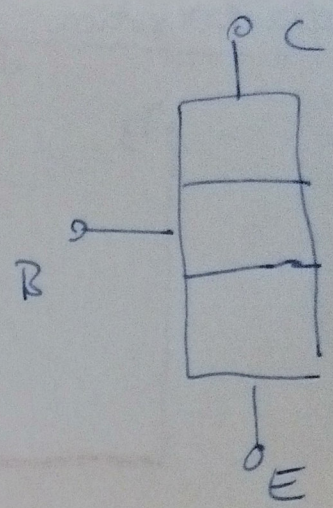


$$V_{CE} \geq 0$$

$$I_C = 0$$

$$V_{BE} < 0.7V$$

$$V_{BE} \approx 0.7V$$

BJT:


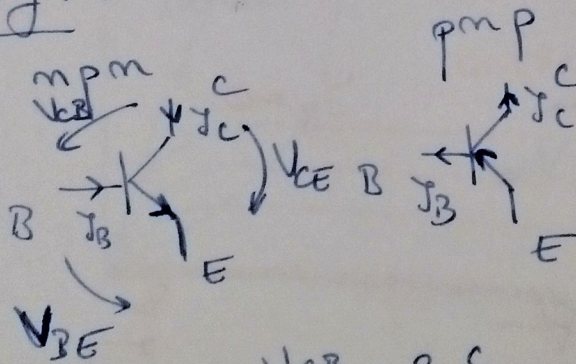


$$I_C \approx mA$$

$$I_B \approx \mu A$$


$$I_E = I_C + I_B$$

$$V_{CB} = V_{CE} - V_{BE}$$

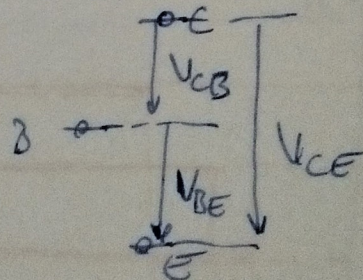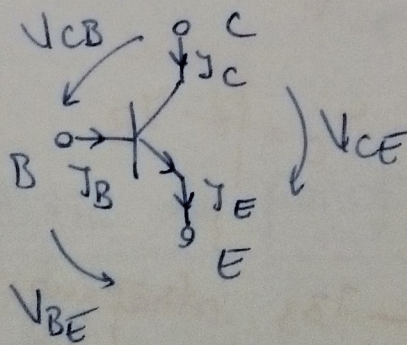


$$I_E \approx I_C$$

Caracteristica jonctiunii BE:


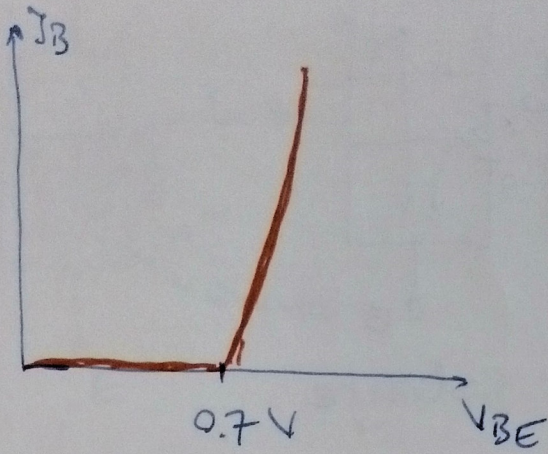


Caracteristicile colectoarei:


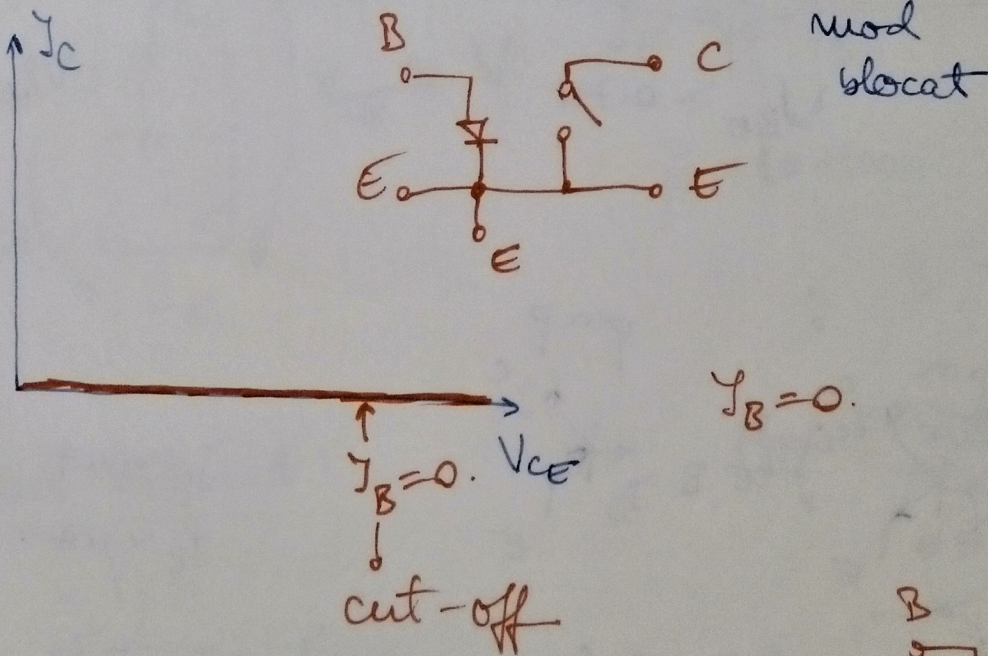


mod activ.

$$I_C = \beta \cdot I_B$$

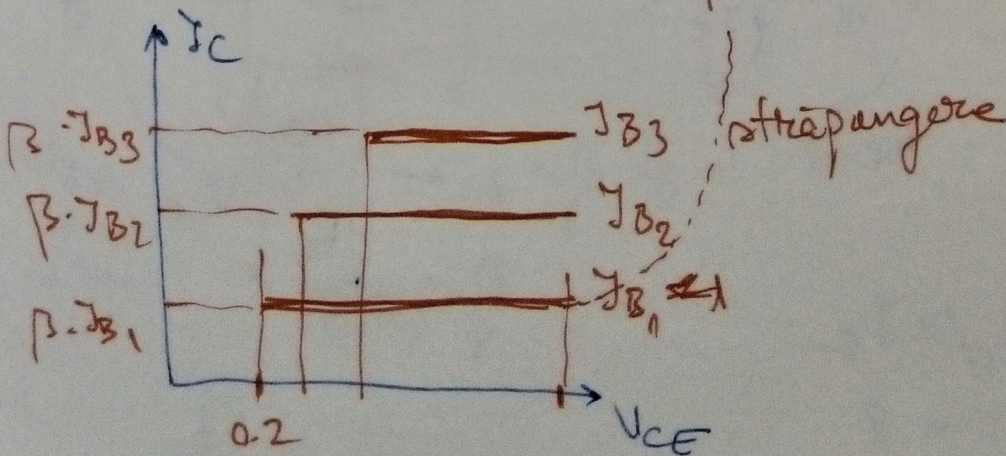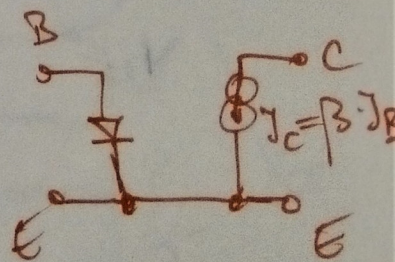


Modul saturat

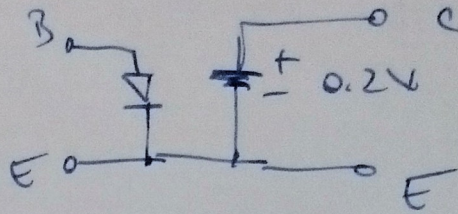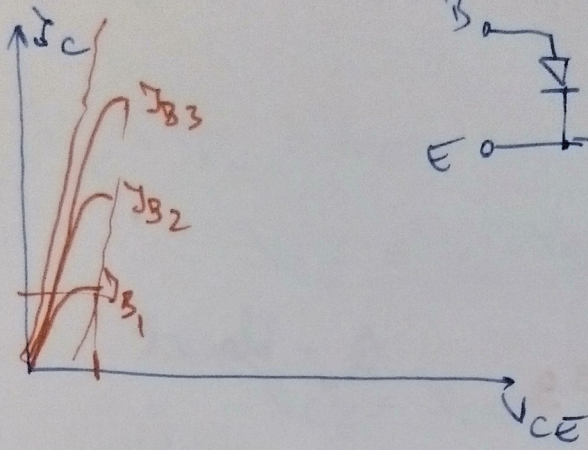




$$P_T = V_{CE} \cdot I_C + \underbrace{V_{BE} \cdot I_B}$$

$$P_T \approx V_{CE} \cdot I_C$$

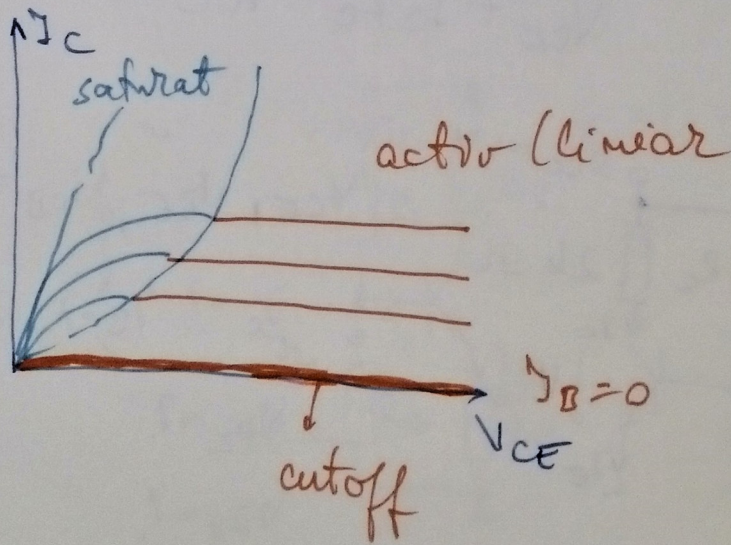

Punctul static de functionare al TB.

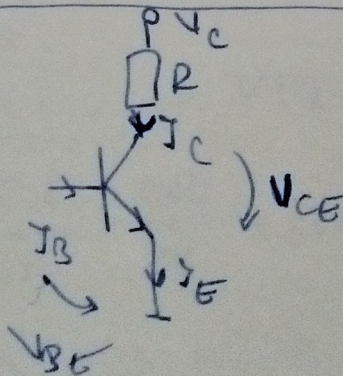


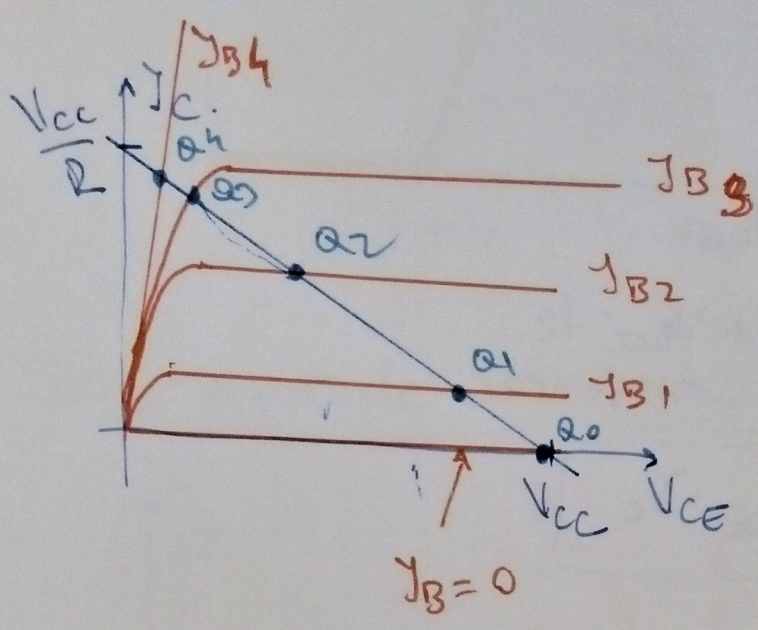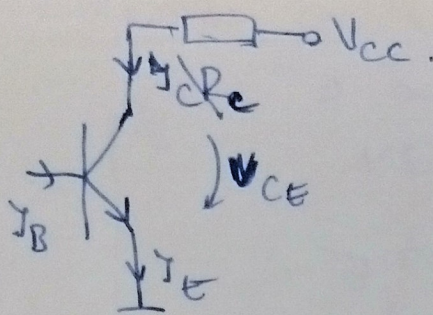

Q_0 - blocat
 Q_1, Q_2 - activ.
 Q_3, Q_4 - saturat

$$V_{CE} + I_C R_C = V_{CC}$$

(1)

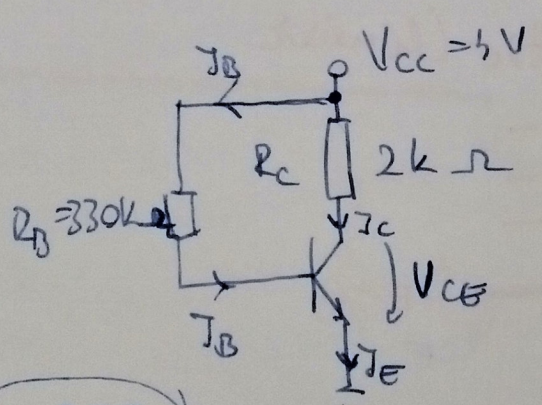

$V_{CE}, V_{BE}, V_{CB} = ?$
 $I_C = ?$ $I_B = ?$ $I_E = ?$
 $V_{RC} = ?$
 $V_{RB} = ?$

$\beta = 100$

$$V_{BE} \approx 0.7 \text{ V}$$

$$I_C = \beta \cdot I_B = 100 \cdot 10 \mu\text{A} = 1 \text{ mA}$$

$$V_{RB} = V_{CC} - V_{BE} = 4 - 0.7 = 3.3 \text{ V}$$

$$V_{RB} = I_B \cdot R_B \Rightarrow I_B = \frac{V_{RB}}{R_B} = \frac{3.3 \text{ V}}{330 \cdot 10^3 \Omega} =$$

$$= \frac{3.3}{330} \text{ mA} = 0.01 \text{ mA} = 10 \mu\text{A}$$

(6)

$$V_{Rc} = I_c \cdot R_c = 1 \text{ mA} \cdot 2000 \Omega = 2000 \text{ mA} \cdot \Omega = 2 \text{ V}$$

$$V_{cc} = V_{Rc} + V_{ce}$$

$$V_{ce} = V_{cc} - V_{Rc} = 4 - 2 = 2 \text{ V}$$

$$V_{cb} = V_{ce} - V_{be} = 2 - 0.7 = 1.3 \text{ V}$$


(P10)

$$\beta = 100$$

$$R_1, R_c, R_E \quad I_c = 2 \text{ mA}$$

$$I_B = ? \quad V_{ce} = 3 \text{ V}$$

$$V_{be} = 0.65 \text{ V}$$

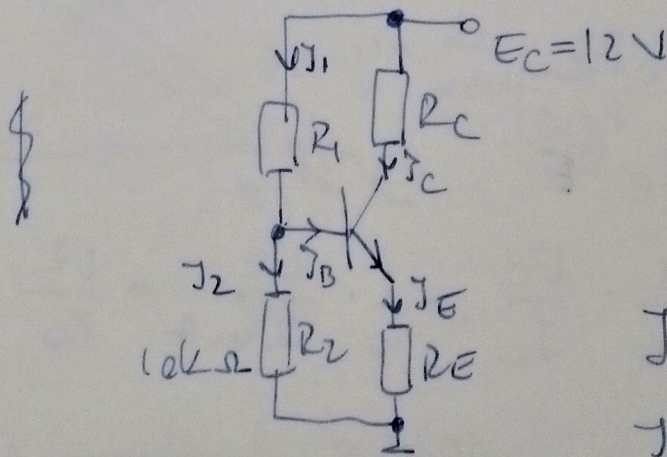

$$I_c = \beta \cdot I_B$$

$$I_B = \frac{I_c}{\beta} = \frac{2 \text{ mA}}{100} = 20 \mu\text{A}$$

$$V_{R2} = V_{be} = 0.65$$

$$12 = V_{R1} + 0.65 \quad V_{R1} = 11.35 \text{ V}$$

$$I_1 = I_2 + I_B$$

$$I_1 = 65 + 20 \mu\text{A} = 85 \mu\text{A}$$

$$V_{R2} = I_2 R_2 \Rightarrow 0.65 = I_2 \cdot 10 \text{ k}\Omega$$

$$I_2 = \frac{0.65}{10.000} = 65 \mu\text{A}$$

(7)

$$U_{R_1} = I_1 \cdot R_1 = 85 \mu\text{A} \cdot R_1$$

$$11.35\text{V} = 85 \mu\text{A} \cdot R_1$$

$$R_1 = \frac{11.35}{85} \cdot 10^6 = \frac{11.35}{85} \cdot 10^6 \approx 133 \text{ k}\Omega$$

$$R_1 = \frac{11.35}{85} \cdot 10^6 = 0.133 \cdot 10^6 \Omega = \underline{\underline{133 \text{ k}\Omega}}$$

$$I_E = I_C + I_B = 2 \text{ mA} + 65 \mu\text{A} = 2 + 0.065 \text{ mA} = 2.065 \text{ mA}$$

$$I_C = 2 \text{ mA}$$

$$U_{CE} + U_{R_C} + U_{R_E} = 12 \text{ V}$$

$$U_{R_C} = I_C R_C$$

$$U_{R_E} = I_E R_E$$

$$R_E \approx \frac{1}{10} \cdot \frac{E_C}{I_C} = \frac{1}{10} \cdot \frac{12}{2 \text{ mA}} = \frac{12}{20} \cdot 10^3 = 600 \Omega$$

$$U_{R_E} = R_E \cdot I_E = 600 \cdot 2.065 = 1.239 \text{ V}$$

$$E_C = U_{R_C} + U_{CE} + U_{R_E}$$

$$12 = U_{R_C} + 3 + 1.239 = 7.761 \text{ V} = I_C R_C =$$

$$= 2 \text{ mA} \cdot R_C$$

ТЕМА: 11, 12, 13.

$$R_C = \frac{7.761}{2} \cdot 10^3 = 3.88 \text{ k}\Omega$$