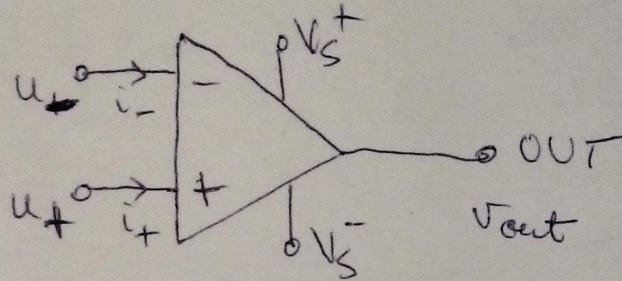


Amplificatorul operational

AO → c.i.



AO IDEAL:

$$v_{out} = A_d (u_+ - u_-)$$

Ad - open-loop gain

$$A_d = \infty \quad i_+, i_- = 0$$

$$Z_{in} = \infty$$

$$Z_{out} = 0$$


A.O REAL:

$$A_d = 2 \cdot 10^5$$

$$Z_{in} = 10^6 \Omega$$



$$Z_{out} = 10^2 - 10^3 \Omega$$

$$i_+, i_- = 10^{-12} - 10^{-9} A$$

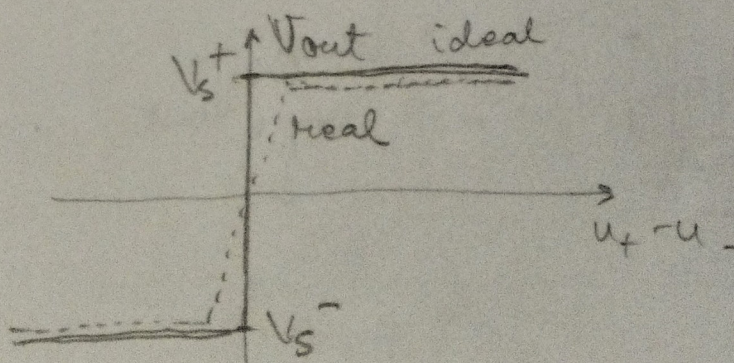


Reacția :


- reacție pozitivă

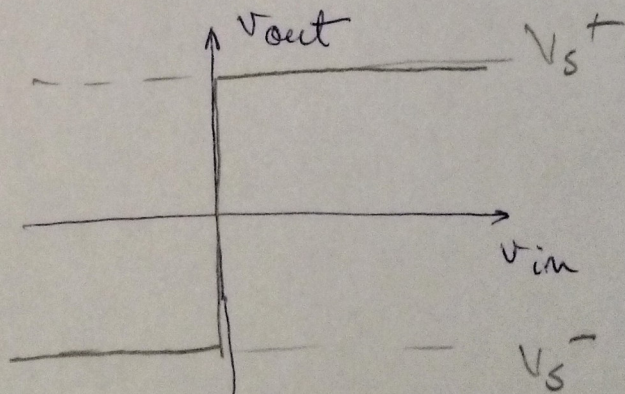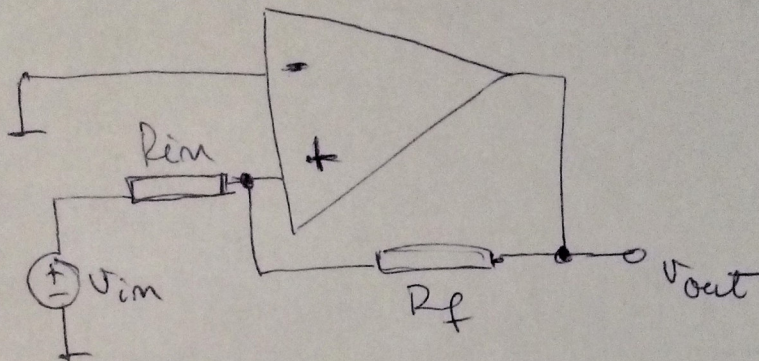

- reacție negativă :

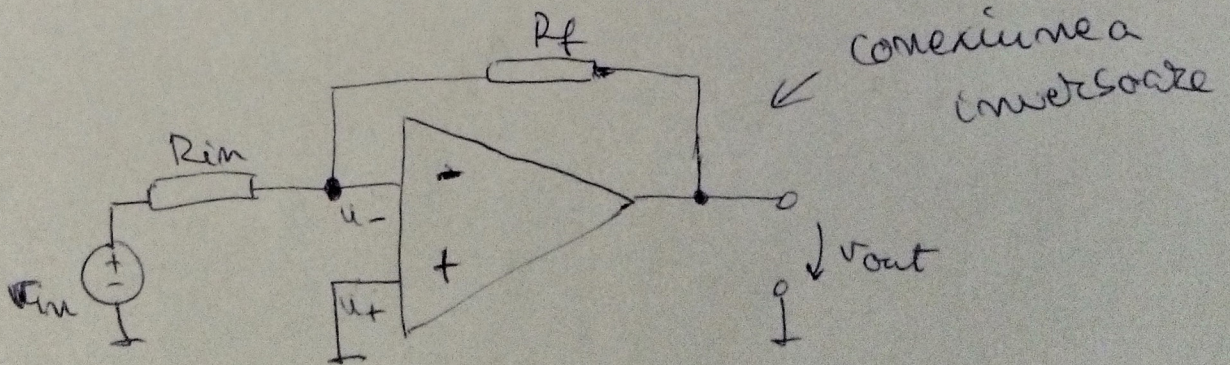

$$u_+ = 0$$

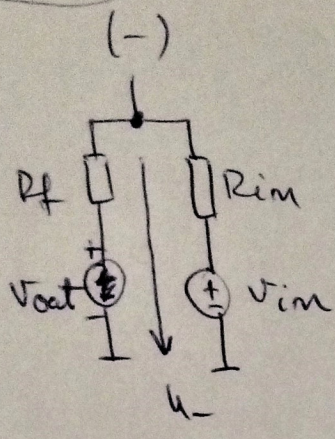

$$u_- = \frac{v_{im}}{R_{im}} + \frac{v_{out}}{R_f} = \frac{1}{R_{im}} + \frac{1}{R_f}$$

$$= \frac{R_f v_{im} + R_{im} v_{out}}{R_{im} R_f} = \frac{R_{im} + R_f}{R_{im} R_f}$$

$$= \frac{R_f v_{im} + R_{im} v_{out}}{R_{im} + R_f}$$

$$u_- = \frac{R_f v_{im} + R_{im} \left(-\frac{R_f}{R_{im}} v_{im}\right)}{R_{im} + R_f} = 0$$

$$v_{out} = A_{ol} (u_+ - u_-) = A_{ol} \left(0 - \frac{R_f v_{im} + R_{im} v_{out}}{R_{im} + R_f}\right)$$

$$v_{out} = - \frac{A_{ol} (R_f v_{im} + R_{im} v_{out})}{R_{im} + R_f}$$

$$v_{out} (R_{im} + R_f) = -A_{ol} R_f v_{im} - A_{ol} R_{im} v_{out}$$

$$v_{out} (R_{im} + R_f + A_{ol} R_{im}) = -A_{ol} R_f v_{im}$$

$$v_{out} = - \frac{A_{ol} R_f v_{im}}{R_{im} A_{ol} + R_{im} + R_f} =$$


$$= - \frac{A_{ol} R_f v_{im}}{A_{ol} \left(R_{im} + \frac{R_{im} + R_f}{A_{ol}}\right)}$$

$$v_{out} = - \frac{R_f}{R_{im} + \frac{R_{im} + R_f}{A_{ol}}} \cdot v_{im} \Rightarrow$$

$$v_{out} = - \frac{R_f}{R_{im}} \cdot v_{im}$$


↓
A_{inv}

- comenirea memorsoare:

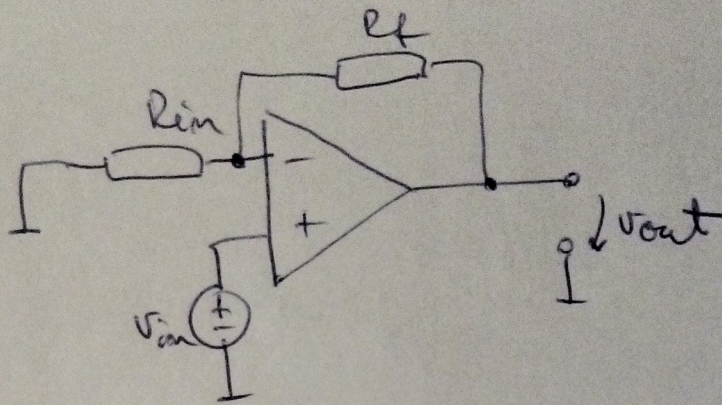

~~u_+ = v_in~~
 $u_+ = v_{in}$
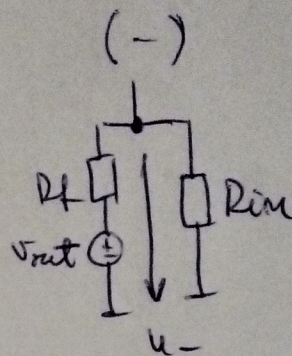
$$u_- = \frac{\frac{v_{out}}{R_f} + \frac{0}{R_{in}}}{\frac{1}{R_f} + \frac{1}{R_{in}}} =$$





$$= \frac{\frac{v_{out}}{R_f}}{\frac{R_{in} + R_f}{R_{in} R_f}} \Rightarrow u_- = \frac{v_{out} \cdot R_{in}}{R_{in} + R_f}$$


$$u_+ = u_- \Rightarrow \frac{v_{out} R_{in}}{R_{in} + R_f} = v_{in} \Rightarrow$$

$$\Rightarrow v_{out} = \frac{R_{in} + R_f}{R_{in}} \cdot v_{in} = \underbrace{\left(1 + \frac{R_f}{R_{in}}\right)}_{\text{Ameinw.}} v_{in}$$

- conexiunea diferențială -

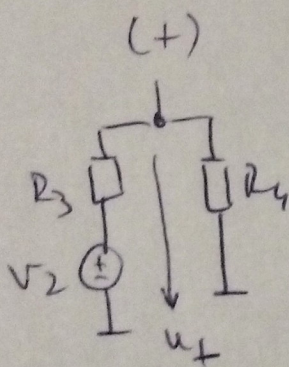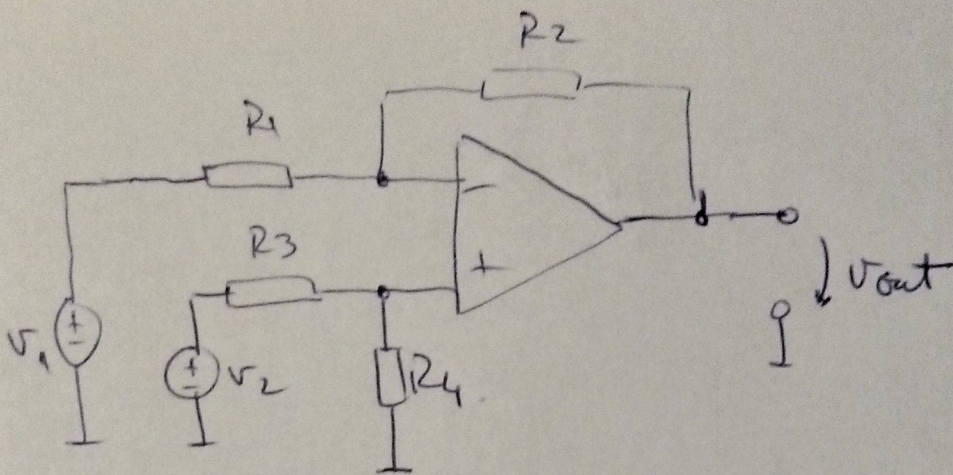
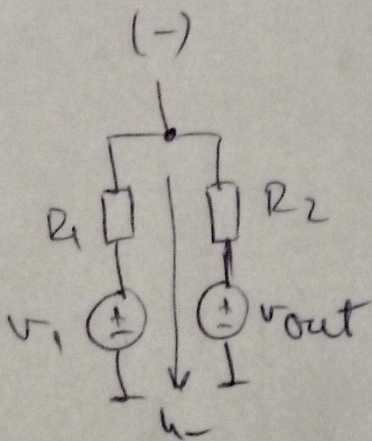
$$u_+ = \frac{\frac{v_2}{R_3} + \frac{0}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}} = \frac{\frac{v_2}{R_3}}{\frac{R_3 + R_4}{R_3 R_4}} = \frac{v_2 R_4}{R_3 + R_4}$$



$$u_- = \frac{\frac{v_{out}}{R_2} + \frac{v_1}{R_1}}{\frac{1}{R_2} + \frac{1}{R_1}} = \frac{\frac{v_{out} R_1 + v_1 R_2}{R_1 R_2}}{\frac{R_1 + R_2}{R_1 R_2}} = \frac{v_{out} R_1 + v_1 R_2}{R_1 + R_2}$$

$$u_+ = u_- \rightarrow \frac{v_2 R_4}{R_3 + R_4} = \frac{v_{out} R_1 + v_1 R_2}{R_1 + R_2}$$

$$v_{out} R_1 + v_1 R_2 = \frac{R_1 + R_2}{R_3 + R_4} \cdot v_2 R_4$$

$$v_{out} R_1 = \frac{R_1 + R_2}{R_3 + R_4} \cdot v_2 R_4 - v_1 R_2$$

$$V_{out} = \frac{R_1 + R_2}{R_3 + R_4} \cdot V_2 \cdot \frac{R_4}{R_1} - V_1 \cdot \frac{R_2}{R_1}$$

$$R_3 = R_1$$


$$R_4 = R_2$$

$$V_{out} = V_2 \cdot \frac{R_2}{R_1} - V_1 \cdot \frac{R_2}{R_1}$$

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$


↓
A_{dif}

- conexiunea sumatoare:

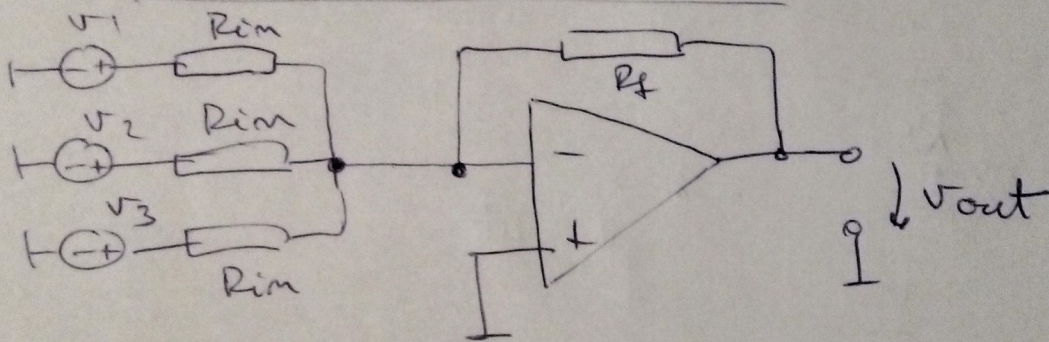

$$u_+ = 0$$

(-)

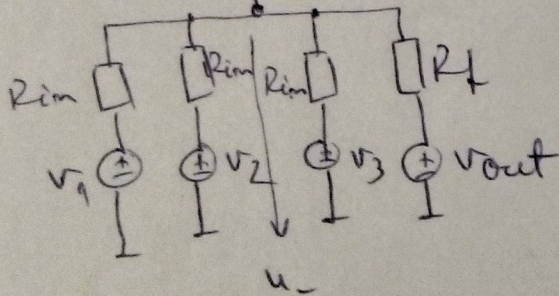

$$u_- = \frac{\frac{V_1}{R_{in}} + \frac{V_2}{R_{in}} + \frac{V_3}{R_{in}} + \frac{V_{out}}{R_f}}{\frac{1}{R_{in}} + \frac{1}{R_{in}} + \frac{1}{R_{in}} + \frac{1}{R_f}} = \frac{R_f (V_1 + V_2 + V_3) + R_{in} V_{out}}{3R_f + R_{in}}$$

$$= \frac{R_{in} R_f}{R_{in} R_f}$$


$$u_+ = u_- \Rightarrow R_f (V_1 + V_2 + V_3) + R_{in} V_{out} = 0$$

$$V_{out} = -\frac{R_f}{R_{in}} (V_1 + V_2 + V_3)$$


(6)

- conexiunea repetitoare :

"buffer", "voltage follower"

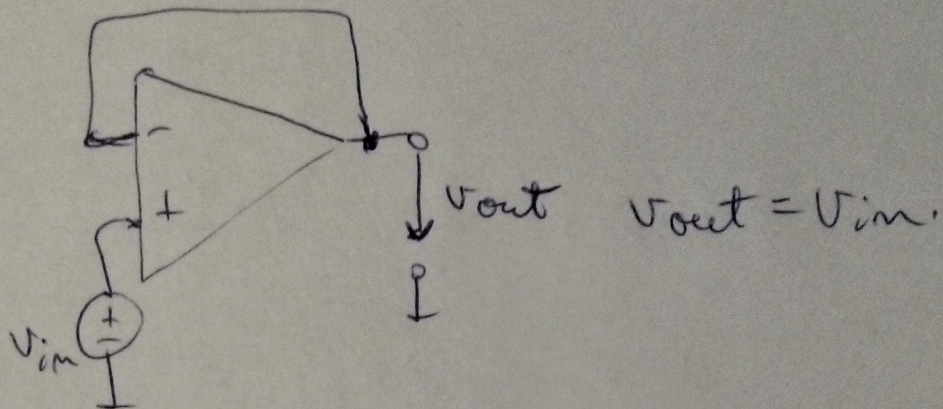

- conexiunea integratoare :

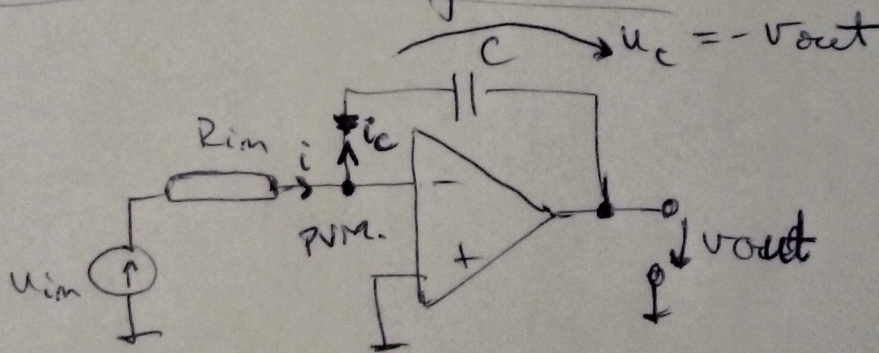

$$\bar{i} = i_c$$

$$i_c = C \cdot \frac{d u_c}{dt} = C \cdot \frac{d(-V_{out})}{dt}$$


$$\bar{i} = \frac{U_{in}}{R_{in}}$$

$$\frac{U_{in}}{R_{in}} = -C \cdot \frac{dV_{out}}{dt}$$


$$V_{out} = - \frac{1}{R_{in}C} \int U_{in} dt$$

1) input bias current:

AO cu TB \sim mA
 AO cu TEG \sim μ A

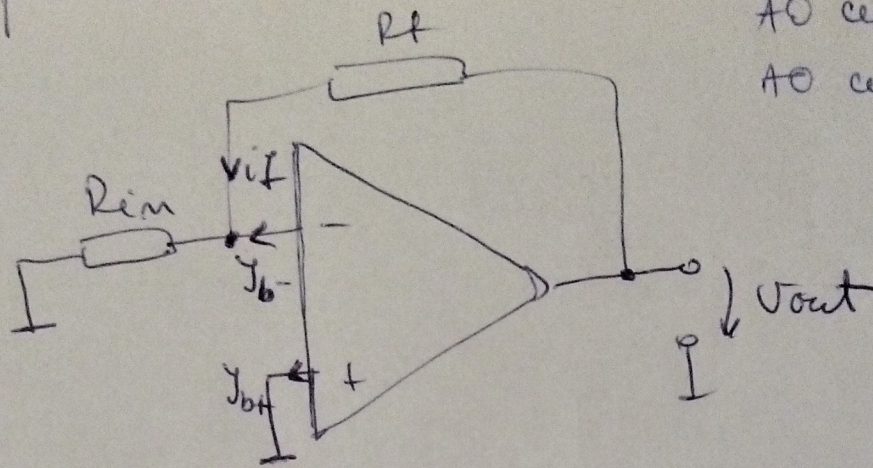

$$V_{out} = I_{b-} \cdot R_f$$

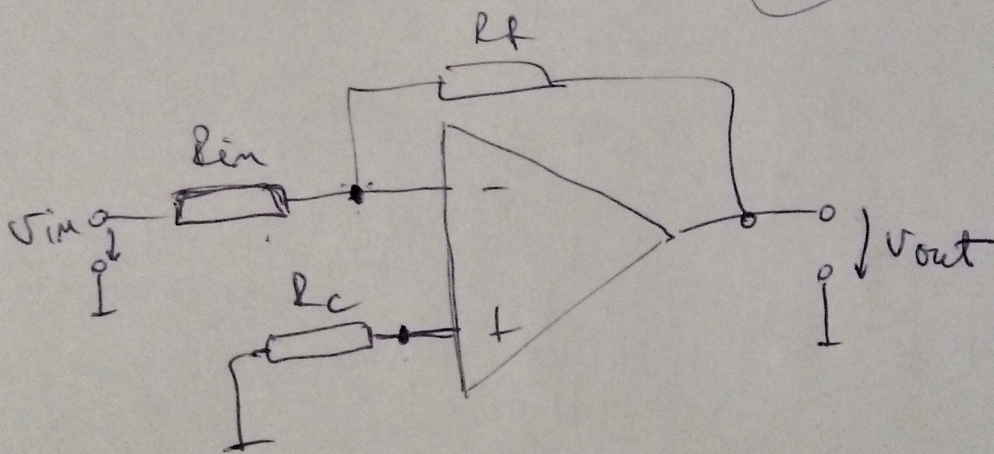


$$R_c = R_{in} \parallel R_f$$

$$V_{in} = 0 \rightarrow V_{out} = I_{off} \cdot R_f = (I_{b+} - I_{b-}) \cdot R_f$$

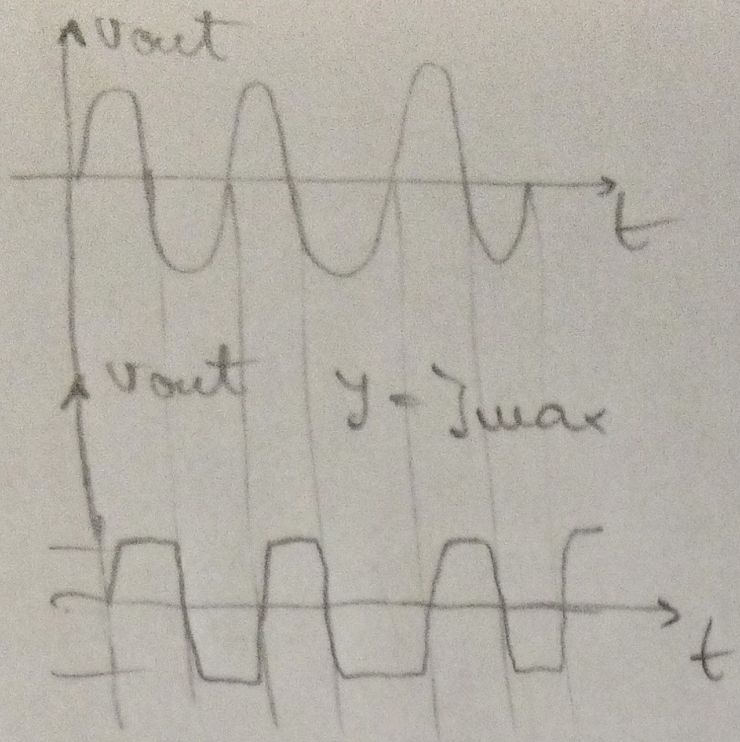2) Slew rate:

$$f_{max} = \frac{\text{slew rate}}{2\pi \cdot V_{max}}$$



Common-mode rejection ratio:

$$CMRR = \frac{A_d}{A_{cm}} \text{ [dB]}$$

Banda de trecere :

